

Charlie Hughes
May 11, 2007

Impedance Measurement

To determine the input impedance of a device both the voltage across the device and the current flowing into the device must be known. The impedance is simply the voltage across the device, E , divided by the current flowing into it, I . This is given by the following equation

$$Z = E / I \quad \text{(Equation 1)}$$

It should be understood that since the voltage, E , and the current, I , are complex quantities the impedance, Z , is also complex. That is to say impedance has a magnitude and an angle associated with it.

When measuring loudspeaker input impedance it is common today for many measurements to be made a relatively low drive levels. This is necessitated because of the method employed in the schematic of Figure 1. In this setup a relatively high value resistor, say 1 kohm, is used for R_s . As seen from the input of the DUT, it is being driven by a high impedance constant current source. Had it been connected directly to the amplifier/measurement system output it would in all likelihood, be driven by a low impedance constant voltage source. In both of these cases constant refers to there being no change in the driving quantity (either voltage or current) as a function of frequency or load.

When R_s is much larger than the impedance of the DUT, the current in the circuit is determined only by R_s . If the voltage at the output of the amplifier, V_o , is known this current is easily calculated with the following equation and is constant.

$$I_s = V_o / R_s \quad \text{(Equation 2)}$$

Now that we know the current flowing in the circuit all we need to do is measure the voltage across the DUT and we can calculate its input impedance.

There is nothing wrong with this method. It is limited, as previously mentioned however, in that the drive level exciting the DUT will not be very large due to the large value of R_s . For some applications this may be problematic. Loudspeakers are seldom used at the low drive levels to which we are limited using the above method. It may be advantageous to be able to measure the input impedance at drive levels closer to those used in actual operation.

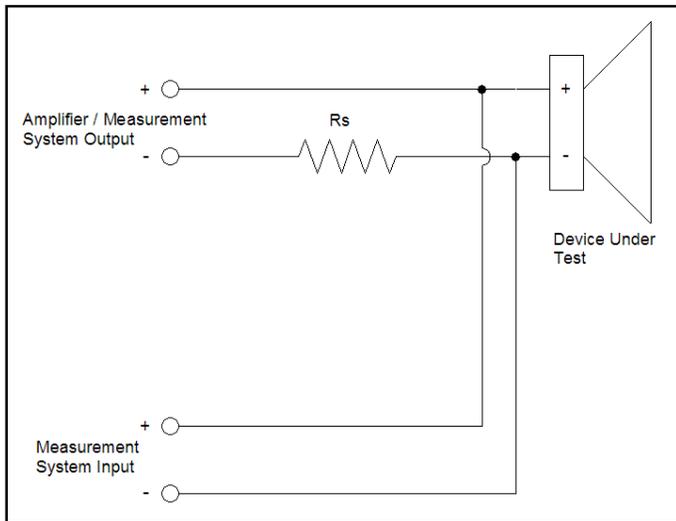


Figure 1 – Schematic of a common method of measuring loudspeaker impedance

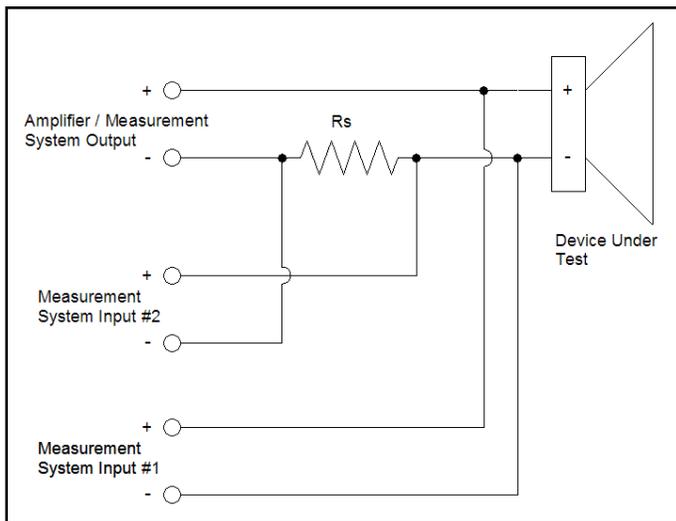


Figure 2 – Schematic of an alternate method of measuring loudspeaker impedance

If the current in the circuit can be measured rather than having to be assumed constant this limitation can be avoided. Using a measurement system with at least two inputs, as shown in Figure 2, can do just that. In this case R_s is made relatively small, say 1 ohm or less. This is called a current sensing resistor. It may also be referred to as a current shunt. Technically this is incorrect for this application as a current shunt is always in parallel with a component from which current is diverted. The voltage drop across R_s is measured by input #2 of the measurement system. The current in the circuit is then calculated using the equation

$$I_s = V_s / R_s \quad (\text{Equation 3})$$

The voltage across the DUT is measured by input #1 of the measurement system. We now know both the voltage across and the current flowing into the DUT so its input impedance can be calculated.

I used EASERA for the measurements in this article. It has facilities for performing all of these calculations as should most dual channel FFT measurement systems. Referencing Figure 2, channel #1 across the DUT should be set as the measurement channel while channel #2 should be set as the reference channel. Dual channel FFT systems divide the measurement channel by the reference channel so we have

$$\begin{aligned} \text{Result} &= \text{Channel \#1} / \text{Channel \#2} \\ &= V_{\text{DUT}} / V_s \end{aligned}$$

By substitution from Equation 3

$$\text{Result} = V_{\text{DUT}} / (I_s * R_s)$$

Since $Z = V_{\text{DUT}} / I_s$ it follows that

$$Z = \text{Result} * R_s \quad \text{or} \quad Z = R_s * \text{Channel \#1} / \text{Channel \#2}$$

All we have to do is multiply our dual channel FFT measurement by the value of R_s used and we get the correct value for impedance. If R_s is chosen to be 1.0 ohm this becomes really easy.

In EASERA there is not an Ohm display selection. Selecting a Volt display will yield the correct values for the displayed curve. For other measurement systems this may work as well, but it is recommended to check the display by measuring a known resistor value for proper calibration.

A very useful device for performing impedance measurements using this current sensing resistor method is the VI Box from LinearX (Photo 1). The signal from the amplifier is routed through the VI Box, which contains the current sensing resistor, and then onto the DUT. It actually contains two selectable sensing resistors, 1 ohm and 10 mohm (milliohm), which allow for measurements using a greater range of current supplied to the load (DUT). The voltage across the selected resistor is present across pins 2 and 3 of one of the XL connectors. The voltage across the DUT is present across pins 2 and 3 of the other XL connector. These connectors allow for quick and easy interface with balanced inputs of a computer/audio interface (sound card). There is also a selectable voltage divider so the input of the audio interface won't be overloaded when testing with very high voltage.

EXCELSIOR AUDIO DESIGN & SERVICES, LLC

2130 Shadwell Court
Gastonia, NC 28056

www.excelsior-audio.com

704.675.5435 Tel
704.675.5436 Fax

Audio & Acoustical Consulting, Design and Measurement



Photo 1 – VI Box from LinearX

I mentioned earlier that measuring input impedance at low drive levels may present a problem for some applications. A couple of these that come to mind are vented loudspeaker enclosures and constant voltage distributed system transformers. I'm sure the interested reader will find others.

The impedance response of a vented loudspeaker enclosure is shown in Figure 3. The angle of the impedance for this device is shown in Figure 4. The vent tuning resonance of this loudspeaker is found when the impedance angle is zero indicating the voltage and current are in phase. This is denoted by the marker at approximate 98 Hz. These graphs show measurements using both the constant current method with a 1 kohm resistor and using a current sensing resistor. The current sensing resistor measurement used a 0 dBV (1.0 V) drive level to excite the loudspeaker. There is some difference between these two measurements. The impedance measurements in Figure 5 tell us much more. In this graph we have additional measurements at +18, +24 and +27 dBV. We can see that at these higher drive levels the impedance curve changes rather dramatically.

The vent surface area of this loudspeaker is relatively small compared to the surface area of the driver. When the woofer is driven harder it moves a lot more air. The vents are too small to allow this same volume of air to be moved through them. The vents saturate. As more air attempts to move through the vents they saturate more and have less of an effect on the loudspeaker response. The impedance response begins to look less like a vented box and more like that of a sealed box.

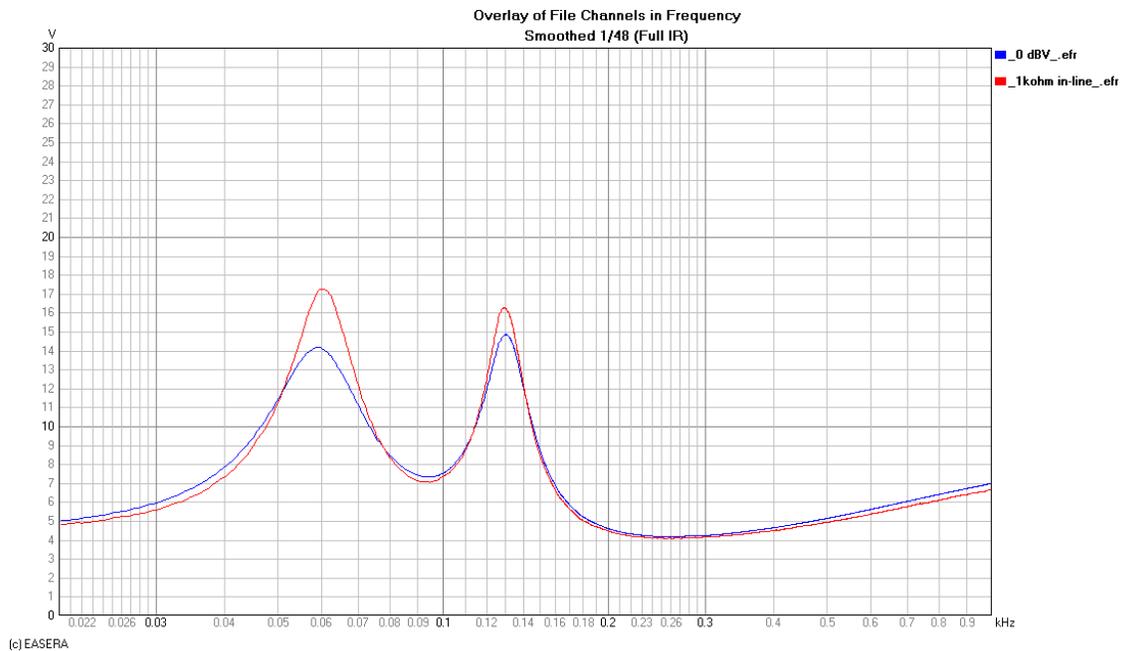


Figure 3 – Impedance of vented loudspeaker measured with a 1kohm resistor (red) & a current sensing resistor at 0 dBV (blue)

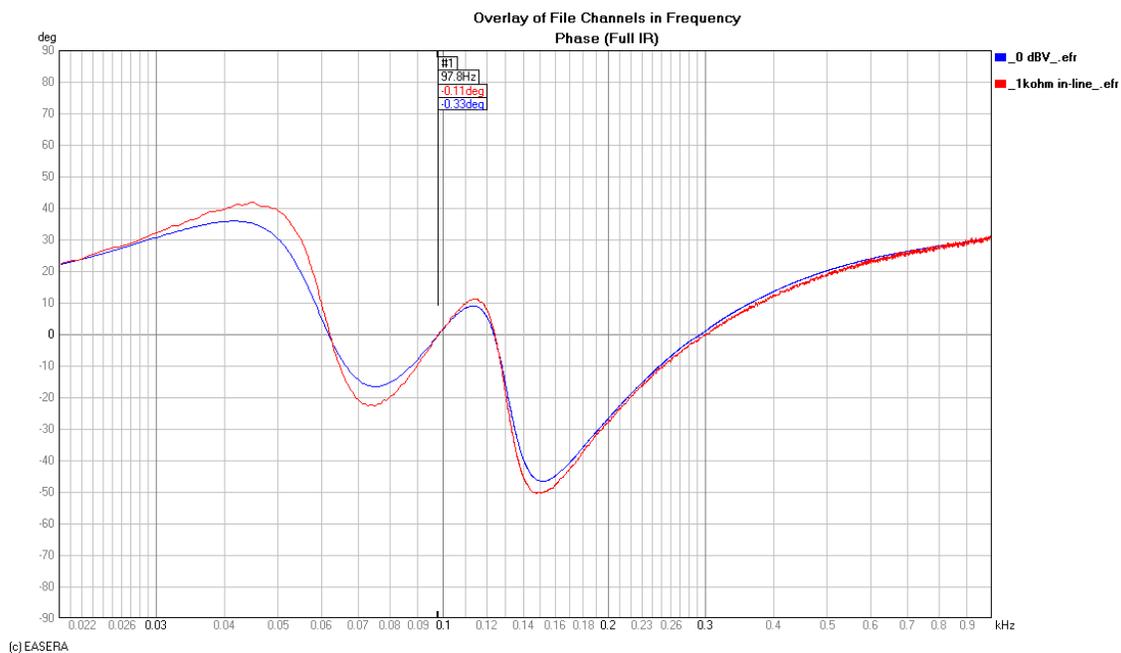


Figure 4 – Impedance angle for vented loudspeaker measured with a 1kohm resistor (red) & a current sensing resistor at 0 dBV (blue)

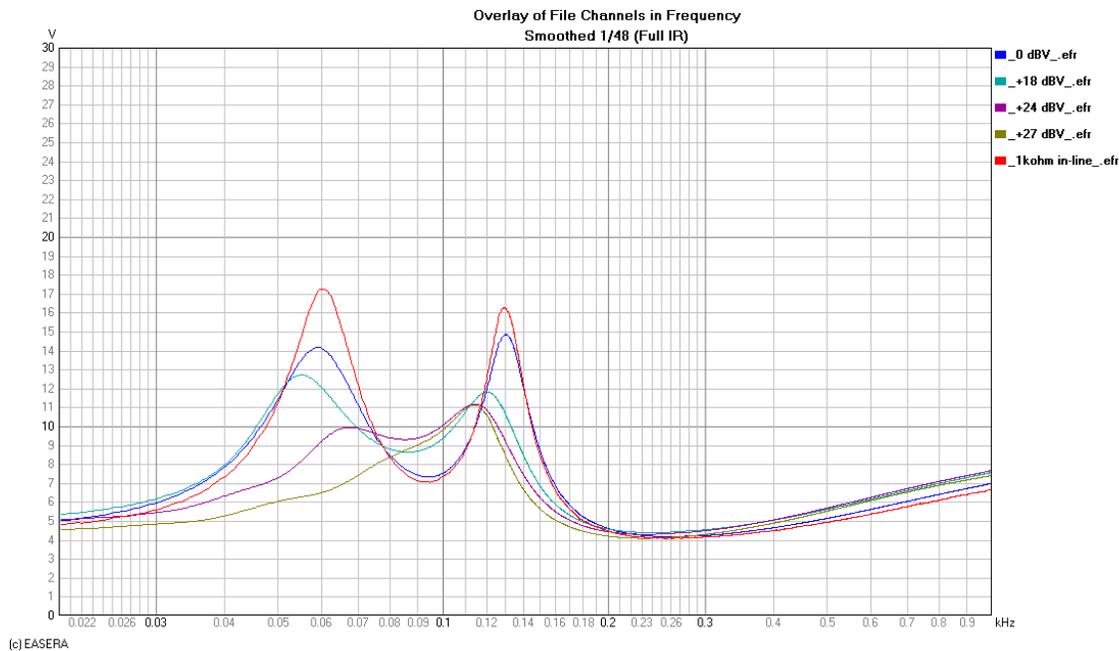


Figure 5 – Impedance of vented loudspeaker measured with a 1kohm resistor & a current sensing resistor at 0, +18, +24 & +27 dBV

A constant voltage distributed loudspeaker system typically requires transformers to be placed immediately in front of the loudspeakers to step down the voltage and step up the current. Testing these types of transformers at low voltage levels typically will not reveal some of the problems that may occur in actual usage. Figure 6 shows the input impedance for each primary tap of a 70.7 V step down transformer with its secondary loaded by an 8 ohm power dissipation test resistor. For each of these measurements the drive voltage was 6.5 V. This is approximately -21 dB from the full rated voltage of 70.7 V. As expected the impedance curves are fairly well behaved.

When driven at 35 V, -6 dB from full rated voltage, there is a problem with the 32 W tap seen in Figure 7. At very low frequencies this transformer does not like being driven at this voltage. The result is that the core saturates. The reflected impedance of the load (on the secondary) as seen by the primary is no longer linear. This violates one of the requirements of the measurement method used (FFT); that the DUT be linear, time invariant (LTI). By placing a second order Butterworth high pass filter in front of the amplifier driving the transformer this core saturation condition can be corrected. A doubling of voltage to 70 V would require the corner frequency of the high pass filter to also be doubled. In this case, the corner frequency should be increased from 30 Hz to 60 Hz.

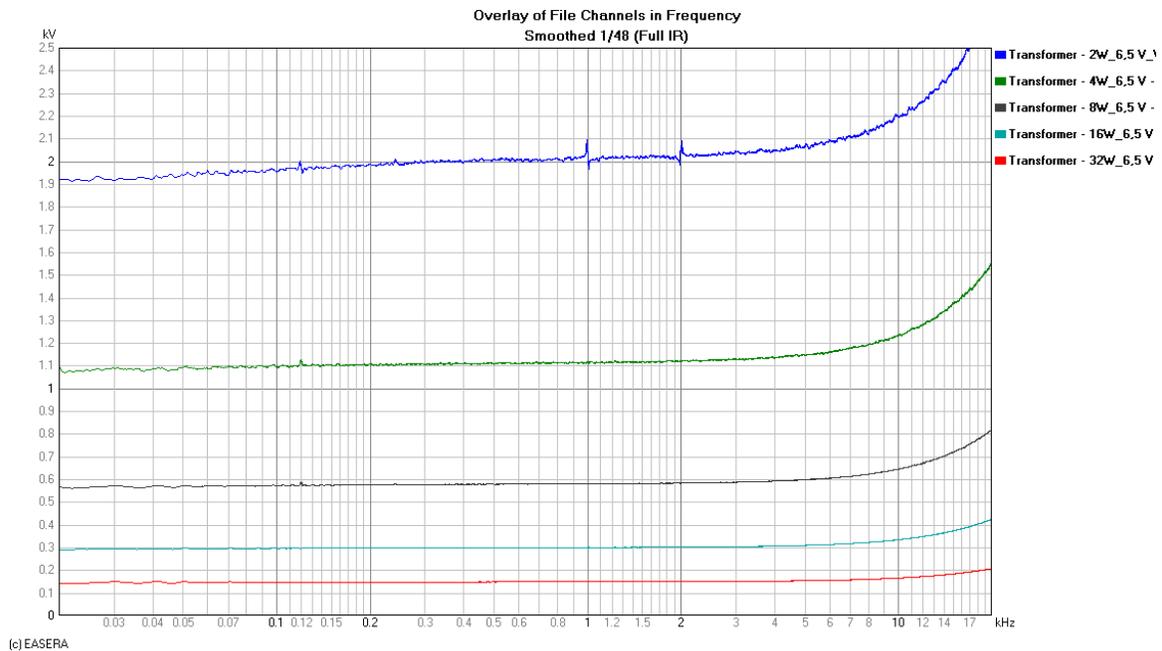


Figure 6 – Impedance of different taps of a 70 V transformer driven at 6.5 V terminated into 8 Ω


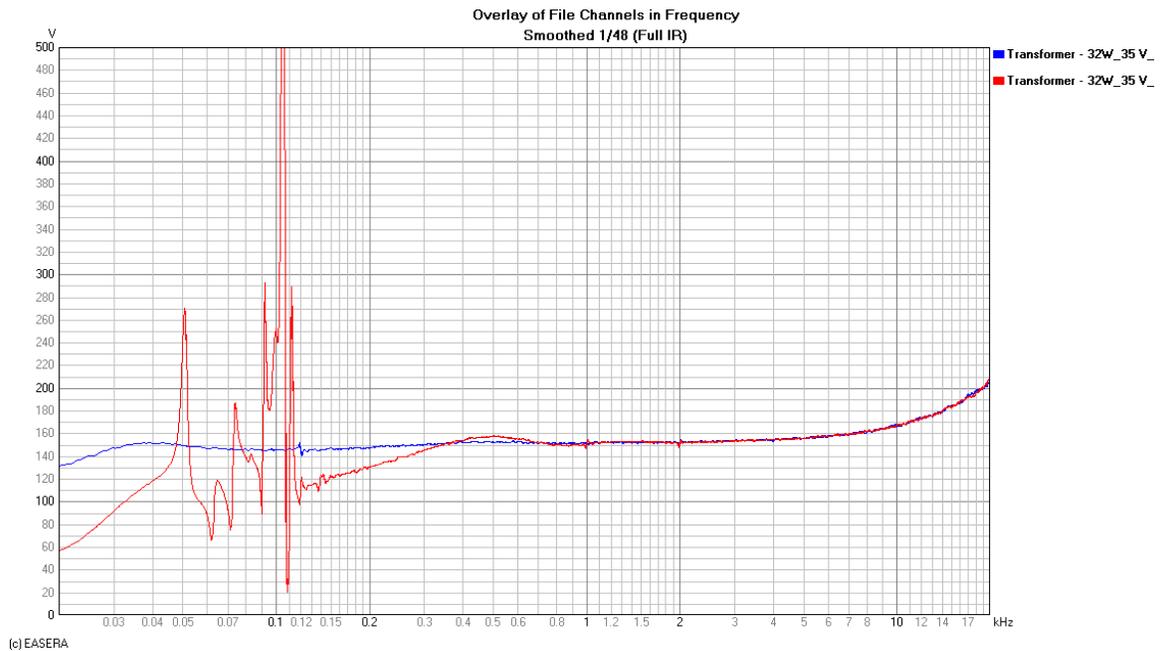


Figure 7 – Impedance of 32 W tap of a 70 V transformer driven at 35 V; 20 Hz HP filter (red), 30 Hz HP filter (blue)

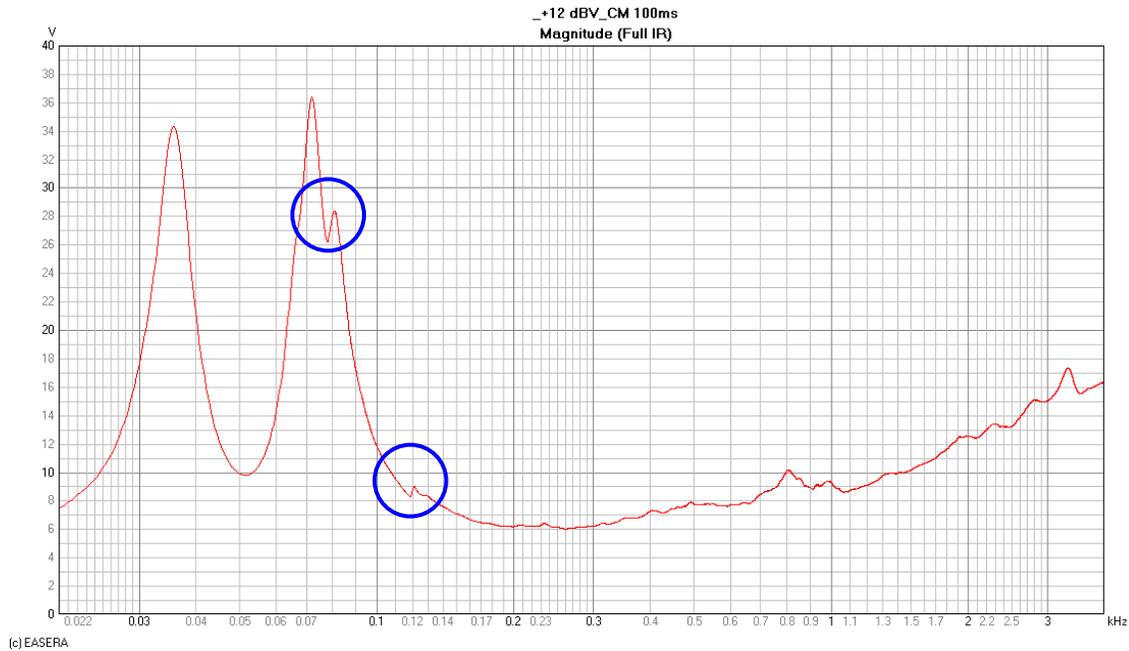

(c) EASERA

Figure 8 – Impedance response of vented loudspeaker

Another use for these types of measurements is to investigate resonance behavior. This can be particularly interesting when viewed as a 3D waterfall. The impedance response of a vented enclosure is shown in Figure 8. There are two features in this graph that should be noted. This is the dip/peak at 80 and 120 Hz. Notice these same frequency regions in Figure 9 & Figure 10. These features don't occur initially. It is only after approximately 60 ms that they become evident. Knowing how long it requires for this resonance to develop may help in determining its cause and implementing a solution.

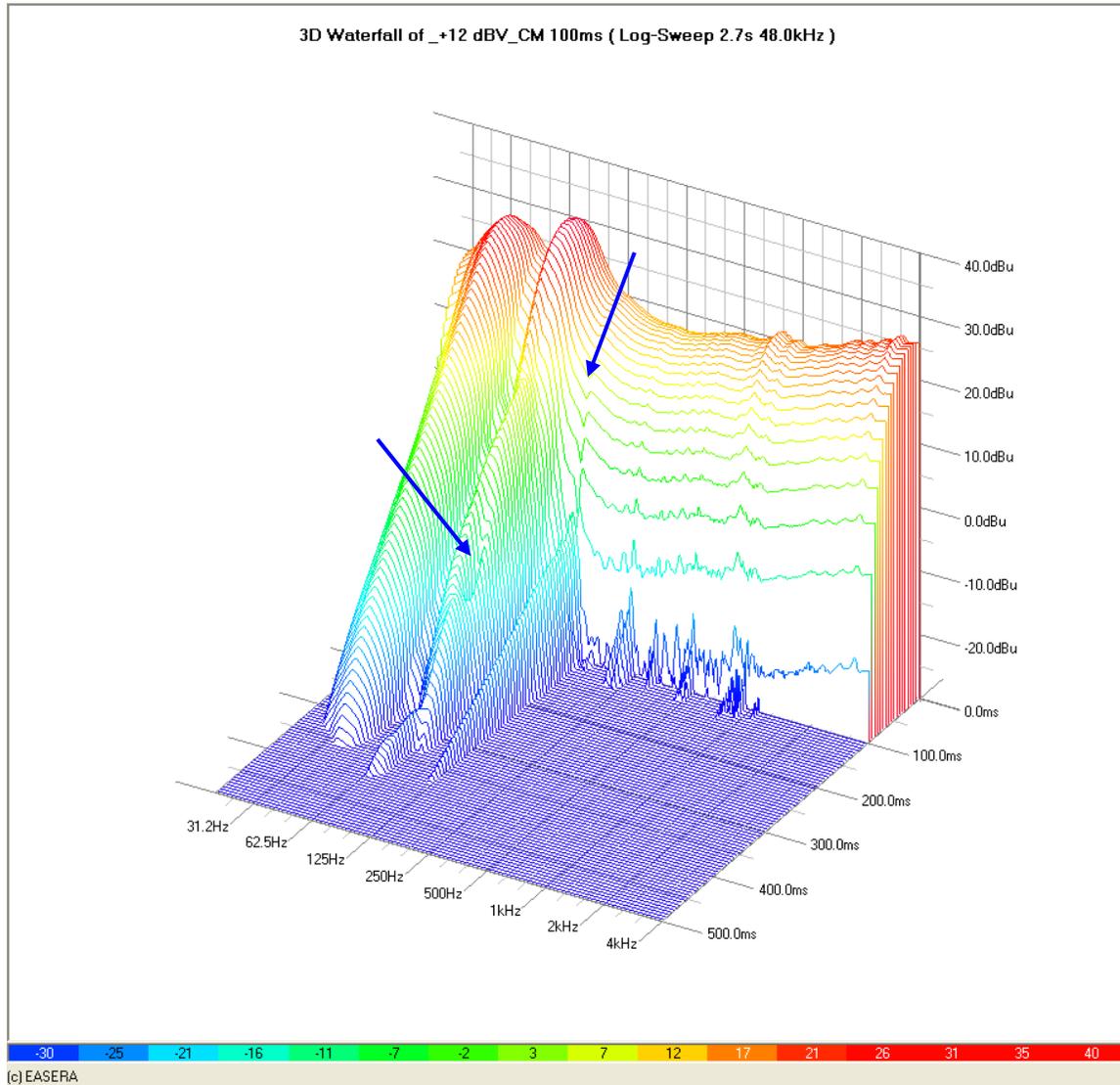


Figure 9 – 3D view of measurement in Figure 8

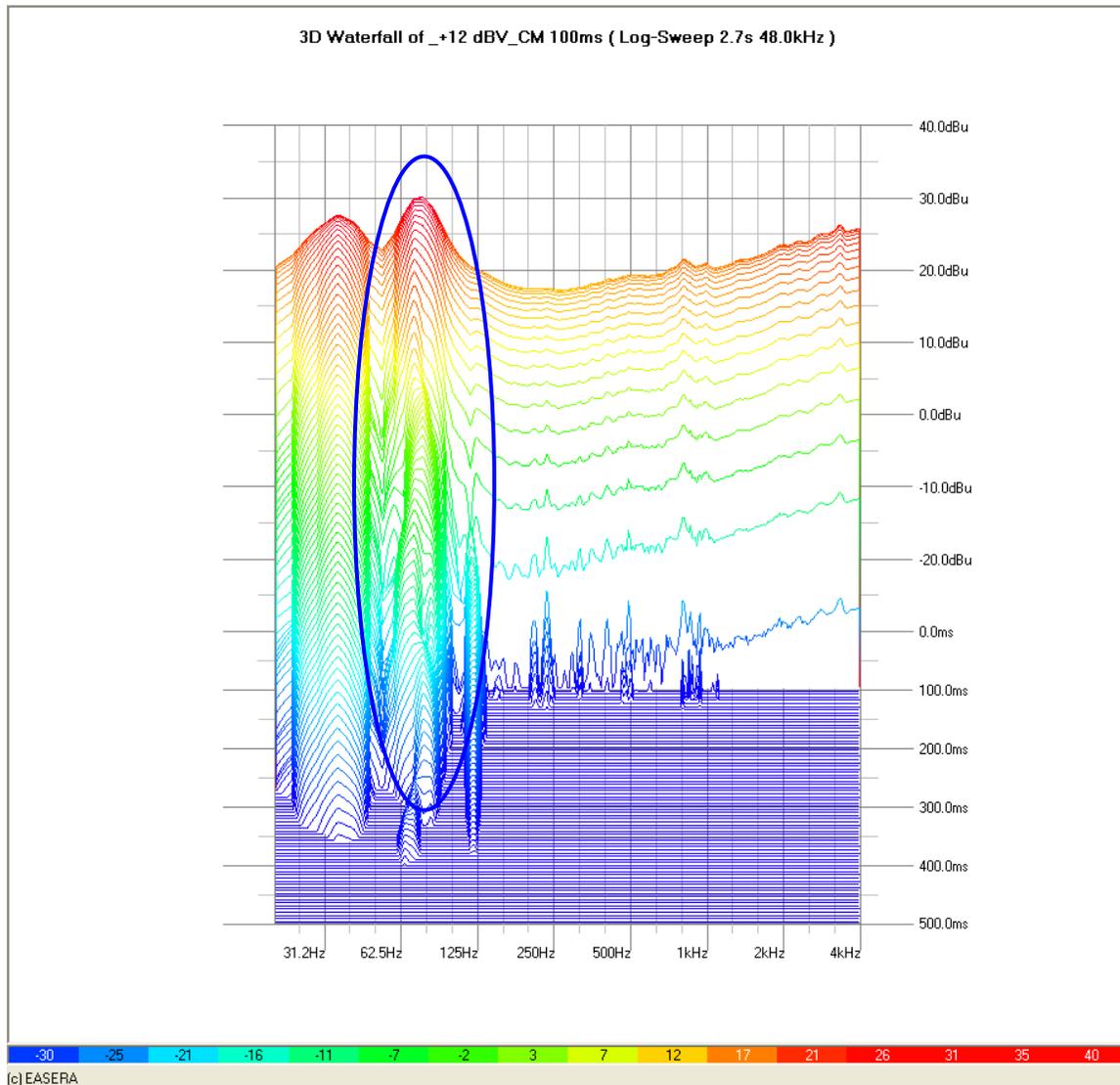


Figure 10 – 3D view of measurement in Figure 8 (note the “wiggling” of the 75 Hz resonance peak)

I hope that the method discussed here to measure impedance at typical application drive level and illustrating some possible uses will be of benefit. Thanks to Jay Mitchell (Frazier Loudspeakers) and Dr. Eugene Patronis (Professor Emeritus, Physics - Georgia Institute of Technology) for their insights on some of these applications.